

Instructions:

- Please turn off and stow away all electronic devices.
 - This is a **closed book and notes** examination. You **may** use the 3-sided reference given to you by the instructor.
 - You have **120 minutes** to complete 120 points. Use your time accordingly.
 - There are 11 problems and 18 pages. Make sure you have the whole exam.
 - To receive partial credit you must show your work. If you believe a question is open to interpretation, then please ask us about it! Please state any assumptions you make.
- Good luck!

Problem	Points	Score
1	0	
2	8	
3	8	
4	12	
5	8	
6	15	
7	12	
8	30	
9	8	
10	13	
11	6	
Total	120	

Your Name _____ NetID _____

1. Write your name here and NetID at the top of each odd page or face -2 pt penalty. [0 pts]

2. Multiple Choice [8 pts]

- (a) [2 pts] **Pipelining.** Consider a non-pipelined processor with clock period C . If you divide the processor into N stages, your new clock period will be:

A less than C/N
 B C/N
 C greater than C/N
 D C
 E N

Your Answer: _____

- (b) [2 pts] **Simple CPU.** Which of the following statements about the Program Counter is false? There is only one correct answer.

A The PC can change every cycle.
 B The PC is a register that has an address in it.
 C The PC is stored in one of the 32 general purpose MIPS registers.
 D The PC always ends in 00.
 E It isn't possible to perform an `addi` instruction that adds an immediate value to the PC.

Your Answer: _____

- (c) [2 pts] **Endian-ness.** Which of the following instructions are endian-independent? (In other words, which of these instructions can be executed correctly without knowing the endian-ness of the machine?) There is only one correct answer.

A Load byte
 B Load halfword
 C Load word
 D None of these instructions are endian-independent.
 E All of these instructions are endian-independent.

Your Answer: _____

- (d) [2 pts] **MIPS.** Which of the following is **not** a way in which MIPS is ideal for pipelining?

A All MIPS instructions are 32 bits.
 B MIPS only has 3 instruction formats.
 C Memory can only be accessed by load and store instructions.
 D Registers can only be accessed by R-type instructions.
 E All of these are ways in which MIPS is ideal for pipelining.

Your Answer: _____

3. Number Systems [8 pts]

- (a) [2 pts] Express the unsigned integer 10010011 in decimal (base 10).

Value in decimal: _____

- (b) [2 pts] Express the sign magnitude number 10010011 in decimal (base 10).

Value in decimal: _____

- (c) [2 pts] Express the 2s complement number 10010011 in decimal (base 10).

Value in decimal: _____

- (d) [1 pt] Express the unsigned binary number 10010011 in octal.


Octal representation: _____

- (e) [1 pt] Express the 2s complement number 10010011 in octal.

Octal representation: _____

4. Transistors, Gates, and Storage [12 pts]

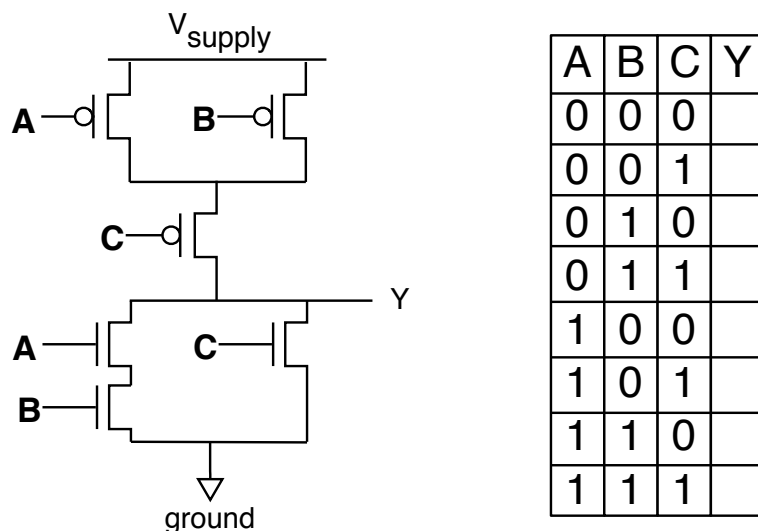
- (a) [4 pts] Recall that a p-transistor connects source to drain when a negative/zero charge is applied to the gate. Complete the truth table for the following CMOS circuit with inputs A, B, and C and output Y.



- (b) [2 pts] DeMorgan's Laws are logical identities that can be used to simplify or manipulate a logical formula. One of them states: $\overline{(ab)} = \bar{a} + \bar{b}$

Draw the circuit version of both sides of this equation. You should draw two distinct (non-identical) circuits that have the same functional behavior. They should both have inputs A and B. They should not be connected to each other. You may use any standard logic gates.

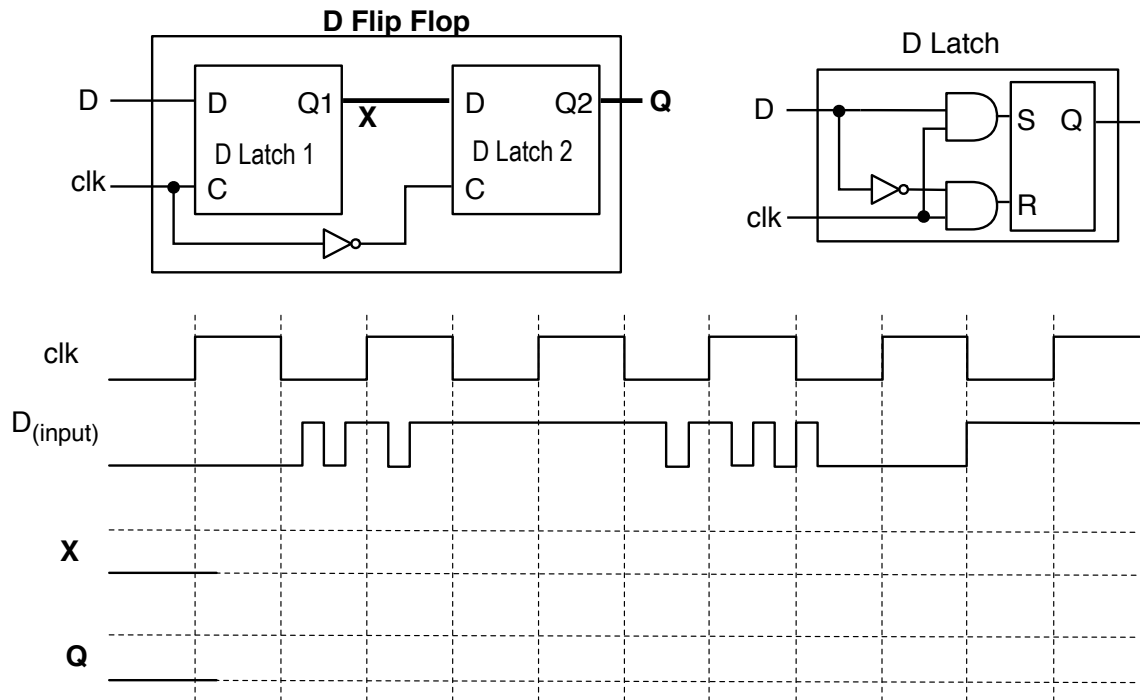
- (c) [6 pts] Complete the timing diagrams, indicating the values for X (the output of the first D Latch) and Q (the output of the D Flip Flop) in the following diagram. Both X and Q start low.



5. Components [8 pts]

Decoders convert a binary input value to a unary (one-hot) output. Another frequently used component is an **encoder** which does the opposite. It takes a unary input and converts it into a binary encoded output. An encoder answers the question “which input was hot?”. A 4-to-2 encoder’s input is in the form $I_3 I_2 I_1 I_0$ and its output is in the form $O_1 O_0$. If you input 0100 into the encoder, the output will be 10, which means “Input I_2 was hot”. You may assume that there are only ever 4 input combinations to the encoder: 1000, 0100, 0010, and 0001 and the encoder only needs to create the correct output for these 4 input combinations.

- (a) [4 pts] Draw the circuit diagram for a 4:2 encoder using basic logic gates with any number of inputs. Use the inputs and outputs provided. The zero indexed bit is the *least significant bit*. You do not need to simplify your circuit. (That comes next).

 
 I_3 —

— O_1
 I_2 —

 I_1 —

— O_0
 I_0 —

- (b) [4 pts] Now simplify and re-draw your circuit using the method of your choice. If your circuit above is already simplified (and correct) then you will be awarded the points for this part with no further work required.

6. Logic Minimization [15 pts]

For this question, you have only inverters, 2-input AND gates, and 2-input OR gates. Assume that these gates have a delay of 1, 2, and 3 ns respectively.

Consider the un-simplified circuit associated with the following logic:

$$\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + \overline{\overline{A} + \overline{BC}} \overline{\overline{BC}}$$

- (a) [3 pts] What is the maximum delay for this circuit? Assume the circuit is implemented as efficiently as possible but **has not been simplified at all**.

- (b) [6 pts] Simplify the above equation using boolean logic. Apply only **one simplification per line** to receive full credit.

$$\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + \overline{\overline{A + (\overline{BC}) (\overline{BC})}} =$$

- (c) [2 pts] What is the maximum delay for your simplified circuit?


- (d) [4 pts] Simplify the function shown in the following Karnaugh map. Your equation must be as simple as possible in order to receive full credit.

		CD			
		00	01	11	10
AB	00	x	1	0	1
	01	x	1	x	1
	11	0	1	1	x
	10	0	1	0	0

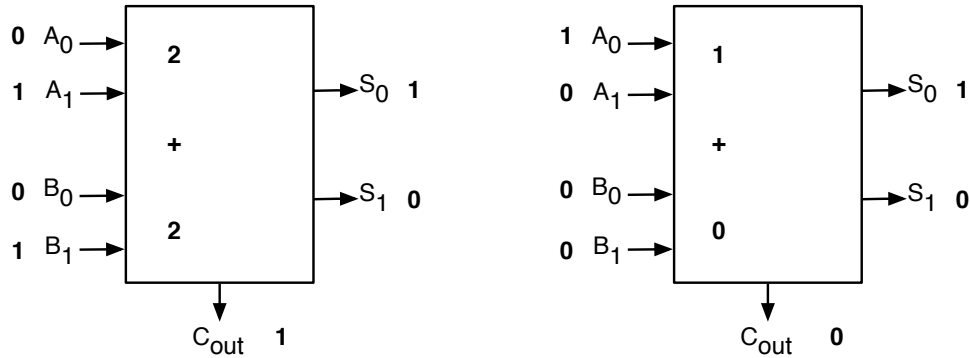7. Arithmetic [12 pts]

A ternary half-adder adds two **base 3** digits together, producing a sum digit and a carry-out bit. To represent ternary digits 0, 1, and 2, we will use bit pairs A_1A_0 with values 00, 01, and 10, respectively. Below are two examples of the ternary half-adder in action. On the left you see the inputs and outputs associated with adding $2+2$. Each 2 is represented by the 2-bit pair 10. The sum, 4 cannot be expressed in a single ternary digit which can only express values 0, 1, and 2. The sum is 1 (represented as 01) and the carry-out is 1. On the right, you see $1 + 0$.

Draw the internal circuit of the ternary half-adder. You may use any standard logic gates with any number of inputs. You do not need to minimize the circuit.



Please draw your circuit on the next page.

Please use the inputs and outputs provided.

A_0 _____

_____ S_0

A_1 _____

_____ S_1

B_0 _____

_____ C_{out}

B_1 _____

8. Finite State Machines [30 pts]

- (a) [12 pts] You must design a finite state machine that reports parity ¹ agreement between inputs A and B. Your FSM takes two inputs, A and B, and generates one output Z. The output Z should be 1 when A and B have both had an even number of 1's as inputs OR when A and B have both had an odd number of 1's as inputs. A sample series of inputs and the expected output is shown below. The first inputs and output combination appear on the far right of the sequence.

A = ...111101

B = ...010100

Z = ...011000

Draw a state transition diagram for this FSM. Remember to label your initial state with a double-circle. **Use a minimal number of states to receive full credit.**

¹The parity of a number is whether it is even or odd.

Consider the following State Transition Table:

Current State		Input	Next State		Output
S_1	S_0	I	S'_1	S'_0	O
0	0	0	1	0	0
0	0	1	1	0	1
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	1	0
1	1	1	1	0	0
1	1	0	1	0	0

(b) [2 pts] The state transition diagram associated with this table:

(a) Must be a Moore Machine.

(b) Must be a Mealy Machine.





Your Answer: _____

(c) Could be either a Moore or a Mealy Machine.

(d) It is not possible to know based on the table provided.

(c) [1 pt] Explain why in *one* sentence.

    (d) [8 pts] Draw the state transition diagram associated with the table. Use the following state encoding **A = 00**, **B = 01**, **C = 10**, **D = 11**.



This is the same State Transition Table from the previous page.

Current State		Input	Next State		Output
S_1	S_0	I	S'_1	S'_0	O
0	0	0	1	0	0
0	0	1	1	0	1
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	1	0
1	1	1	1	0	0
1	1	0	1	0	0

- (e) [2 pts] A TA tells you to use a one-hot state encoding. Specifically, she tells you not to use the encoding **A = 00**, **B = 01**, **C = 10**, **D = 11** but instead **A = 0001**, **B = 0010**, **C = 0100**, **D = 1000**. Complete the State Transition Table given the new encoding:

Current State				Input	Next State				Output
S_3	S_2	S_1	S_0	I	S'_3	S'_2	S'_1	S'_0	O
				0					0
				1					1
				0					0
				1					1
				0					0
				1					0
				1					0
				0					0

Do not overthink this question. There is a reason it's only worth 2 points.

- (f) [4 pts] Provide a Boolean equation for the S'_2 Next State bit. Your equation should be minimized in order to receive full credit.

$$S'_2 =$$

- (g) [1 pt] Typically, the combinational logic for next state calculations is simpler when the states are encoded in a one-hot encoding. This simplicity comes at a small hardware price, however. What is that price?

9. Assembly [8 pts]

BEFORE

Register File		Memory	
r0	0	111	
r1		110	
r2		109	
r3	7	108	
r4		107	x0d
r5		106	x0c
r6		105	x0b
r7	100	104	x0a
		103	
		102	
		101	
		100	

fill these boxes
with **decimal** values

Show the register and memory contents
after executing the following 4 instructions
on a little endian machine:

```
addi r3, r0, 3
sll r7, r3, 2
sw r3, 5(r0)
lw r5, 4(r0)
```

fill these boxes
with **hex** values

Only the part under this line will be graded. Show every known value.

AFTER

Register File		Memory	
r0		111	
r1		110	
r2		109	
r3		108	
r4		107	
r5		106	
r6		105	
r7		104	
		103	
		102	
		101	
		100	

10. Performance [13 pts]

Consider a program with the following dynamic instruction counts being executing on a 1 GHz (1 cycle = 1 ns) processor with the following CPI for each instruction type:

- ALU: 40 million, 1 CPI
- Loads: 30 million, 4 CPI
- Stores: 20 million, 1 CPI
- Branches: 10 million, 2 CPI

(a) [2 pts] What is the CPI of this machine running this program?

You decide that the load-store architecture of this processor is not efficient. You create a new instruction which can add two values found in memory and store the result back in memory. When you re-compile the program, the new instruction mix is:

- MemAdd: 10 million, 5 CPI
- ALU: 30 million, 1 CPI
- Loads: 10 million, 4 CPI
- Stores: 10 million, 1 CPI
- Branches: 10 million, 2 CPI

In other words, 10 million adds, 20 million loads, and 10 million stores have been replaced by 10 million **memAdd** instructions, which take 5 cycles. Supporting the new memAdd instruction slows down the clock; the frequency of the new processor is 500 MHz (0.5 GHz, 1 cycle = 2 ns).

- (b) [5 pts] Which is faster: the original processor or the new processor? (2 pts)
Justify your answer. Be concrete. (3 pts)

- (c) [6 pts] You want to compare the performance of processor A and processor B running program X. For each performance metric below, what must be true in order for this metric to be the correct metric?

To use metric:

The following must apply:

(Check *all* that must apply.)

execution time

- ☐ A & B have the same clock speed.
☐ A & B have the same ISA.
☐ none of the above.

MIPS

- ☐ A & B have the same clock speed.
☐ A & B have the same ISA.
☐ none of the above.

CPI

- ☐ A & B have the same clock speed.
☐ A & B have the same ISA.
☐ none of the above.

11. Storage [6 pts]

Below on the left is the interface for the MIPS register file. It is a dual-read, single-write register file with 32 registers; each register holds a 32-bit word. Next to this interface, draw the interface for a new register file that is a single-read, single-write register file with 64 registers; each register holds a 16-bit word. Make your new interface as detailed as the original.

